

Bangladesh Army University of Engineering & Technology
Dept. of CSE, Course Code: CSE-2215, Course Title: Digital Electronics and Pulse Technique
Full Marks: 10, Time: 30 min., CT 1 (17/09/2024),

- | | | |
|--------|--|----------|
| 1. (a) | Can you explain why ECL is also referred to as CML? | 2 |
| (b) | Draw the basic circuit of ECL and also explain its working principles. | 5 |
| (c) | Write two important characteristics of CML. | 3 |

Batch-16th Class Test: 02 Department: CSE Course Code: CSE-2215

Course Title: Digital Electronics and Pulse Technique Full Marks- 15 Time: 30 Minutes.


Q. No.:

Marks

1 (a) Illustrate clipper and clamper. [CO1, PO1, C2]

5

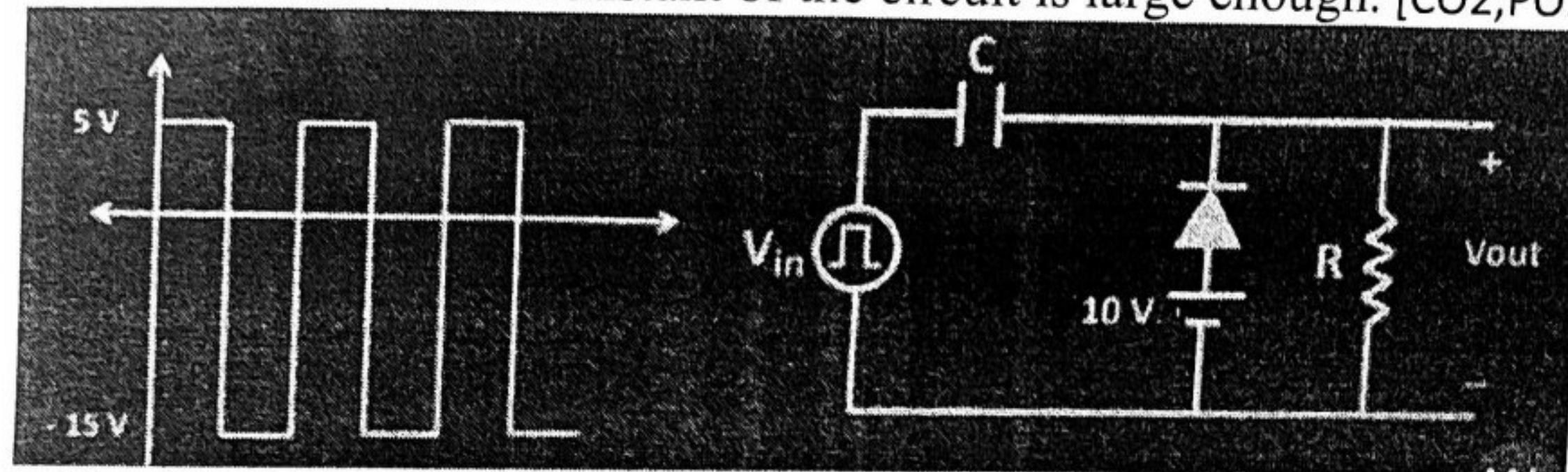(b) For the network shown in below find the output of the waveform. Assume the diode is ideal and the RC time constant of the circuit is large enough. [CO2, PO1, C3]




(c) For the given picture below,

6

i) Identify the circuit.

ii) Calculate V_0

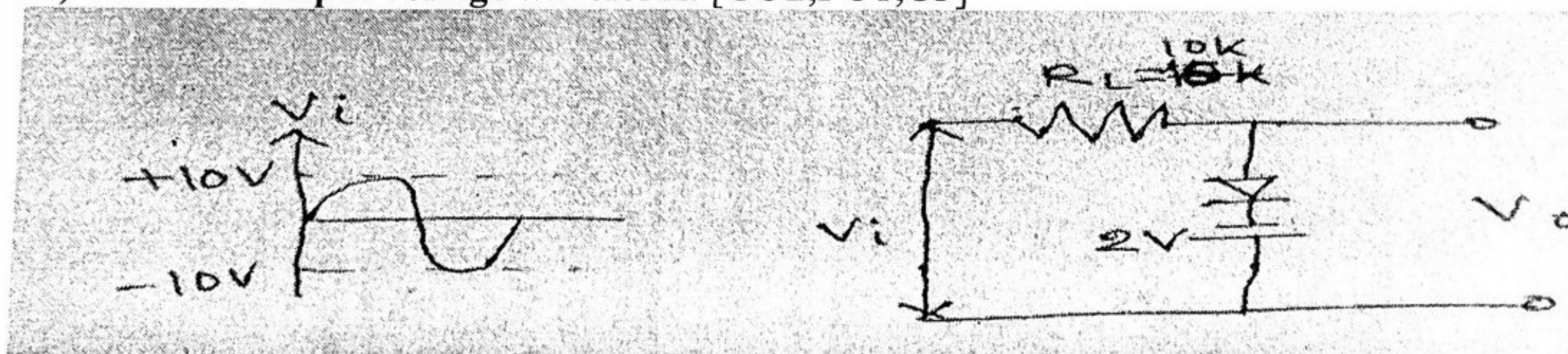iii) Draw the output voltage waveform. [CO2, PO1, C3]



BAUET, CSE, CC: CSE-2215, C T: DEPT, Full Marks: 10, Time: 30 min., CT 2
(05/11/2024).

- | | | |
|--------|---|---|
| 1. (a) | What is FF? Describe the working principle of basic NAND gate FF. | 4 |
| (b) | ^{How} Who would you construct the characteristic equation of clocked RS FF? | 5 |
| (c) | What is the key limitation of JK FF? | 1 |

Batch-16th Class Test: 04 Department: CSE Course Code: CSE-2215

Course Title: Digital Electronics and Pulse Technique Full Marks- 15 Times: 30 Minutes.

Q. No.: 1		Marks
(a)	What function does a DAC perform? Explain the basic characteristics of ADCs. [CO1,PO1,C2]	4
(b)	Assume that the analog sample value is $V_a = 4.4\text{v}$. Show the step by step conversion of the analog sample value 4.4v into digital form by using Successive Approximation ADC. [CO1,PO1,C3]	6
(c)	Show the digital outputs of a 4-bit flash ADC for all the possible sample values of the analog input. [CO1,PO1,C3]	5