

Department of Computer Science & Engineering (CSE)  
B.Sc. Engineering 2<sup>nd</sup> Year 2<sup>nd</sup> Semester Summer-2023

CT-01

Course Code: EEE 2265

Full Marks: 15

Course Title: Electrical Drives and Instrumentation  
Time: 45 Minutes

Answer All the Questions

- |  | Marks |
|--|-------|
| Q.1 Define transformers? Discuss about transformer losses.   | 3     |
| Q.2 A step-up transformer has a turn ratio of 0.5. Transformers' primary current and voltage rated as 10A and 2200V respectively. Transformer's winding parameters are given as $R_p = 15\Omega$ , $X_p = 2.5\Omega$ , $R_s = 25\Omega$ , $X_s = 3\Omega$ . Core resistance, $R_c = 1.5\Omega$ and Magnetizing reactance, $X_M = 2.75\Omega$ . Draw the Exact Equivalent circuit of this transformer referred to the primary side. | 4     |
| Q.3 A shunt dc generator has output current of 450A at 250V output voltage. The shunt field and armature resistances are $50\Omega$ and $0.025\Omega$ respectively. Calculate the armature generated voltage.  | 4     |
| Q.4 A series dc generator has an output voltage of 250V and delivers 15 KW output power. The series field and armature resistances are $0.3\Omega$ and $0.02\Omega$ respectively. Calculate the total armature generated power.  | 4     |

$$P = E_A I_A$$

Department of Computer Science & Engineering (CSE)

B.Sc. Engineering 2<sup>nd</sup> Year 2<sup>nd</sup> Semester Summer-2023

CT-02

Course Code: EEE 2265

Course Title: Electrical Drives and Instrumentation

Full Marks: 15

Time: 45 Minutes

Answer All the Questions

- |     |  | Marks |
|-----|--|-------|
| Q.1 | Define Slip. Draw the power flow diagram of induction motor.   | 3     |
| Q.2 | A 480V, 60 Hz, 50-hp, three phase induction motor is drawing 50A at 0.8 PF lagging. The stator copper losses are 2.5 kW, the rotor copper losses are 700W. The friction and windage losses are 600W, the core losses are 2000W, and the stray losses are negligible. Find (a) The air gap power $P_{AG}$ , (b) The power converted $P_{CONV}$ , (c) Output Power $P_{OUT}$ . | 4     |
| Q.3 | A shunt dc motor has a current load of 400A at 250V terminal voltage. The shunt field and armature resistances are $50\Omega$ and $0.025\Omega$ respectively. Calculate the armature generated voltage.  | 4     |
| Q.4 | A 50-hp, 250V, 1500 r/min dc shunt motor has armature resistances of $0.08\Omega$ , and it produces a no-load speed of 1500 r/min. Find the speed of this motor when its input current is 100A & 200A  | 4     |
- $R_F = 50\Omega$
- $V_t - (I_A \times R_A)$
- $P_{conv} = P_{AG} - P_{rot}$

Department of Computer Science & Engineering (CSE)

B.Sc. Engineering 2<sup>nd</sup> Year 2<sup>nd</sup> Semester Summer-2023

CF-03

Course Code: EEE 2265

Full Marks: 15

Course Title: Electrical Drives and Instrumentation

Time: 45 Minutes

Answer All the Questions

Marks

- Q.1 Draw three bulb connection method of parallel operation of synchronous generator. 3
- Q.2 Draw a circuit diagram of an inverting amplifier. If the  $V_{in} = 10\text{mV}$ , Input resistance  $R_1 = 5\text{k}\Omega$ , feedback resistance  $R_f = 15\text{k}\Omega$ , then find the voltage gain &  $V_o$  for the inverting amplifier. 4
- Q.3 Draw a circuit diagram of a non-inverting amplifier. If the  $V_{in} = 15\text{V}$ , Input resistance  $R_1 = 15\text{k}\Omega$ , feedback resistance  $R_f = 3\text{k}\Omega$ , then find the voltage gain &  $V_o$  for the non-inverting amplifier. 4
- Q.4 Calculate the  $V_o$  and Current  $i_o$  through the resistor  $R_L$  for the following amplifier circuit. 4

